


General Level.

General

- 1) A. 5). D
2). C 6). C
3). C 7). B
4). B 8). E

9). a) Input \rightarrow Process \rightarrow Output.

b) i) 

ii) 

10 

- 11 a).
i). LDR.
ii). Thermistor.
iii). Loudspeaker.

b i) LED, LAMP 7 SEGMENT DISPLAY

b ii). Solenoid, Electric Motor, Relay.

12 a) i). $R = \frac{V}{I} = \frac{6}{0.005} = \underline{\underline{1200 \Omega}}$


- ii). A) LDR \Rightarrow Resistance Decreases
B) Current will Increase.

13 a). Input Output


General

b) i) Thermistor

ii) Loudspeakers

c). 

14 a).

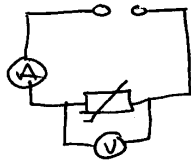

b) i) 18 mA

b) ii) $R = \frac{V}{I} = \frac{5}{0.018} = \underline{\underline{278 \Omega}}$

b) iii). R. decreases. (calc R @ 6V. $R = \frac{6}{0.025} = \underline{\underline{240 \Omega}}$)

15 a). Output Devices: Loudspeakers; LED; CD motor;
7-segment display.

b) Input Devices: On/Off switch; Microphone;

c). electrical \rightarrow light



Electronics - General.

General

16

LDR
Thermistor
Capacitor.

bi). Transistor

ii) Switch. - Electronic Switch.

c) Protect LED from too much current (or Voltage).

A ai) IR detector.

aii). LDR

b) IA) AND

B.

0	0	0
0	1	0
1	0	0
1	1	1

ii). AND.


18. a) Electrical \rightarrow ! Heat \rightarrow Electrical

b). Analogue.

c) i) $I = \frac{V}{R} = \frac{0.8}{500} = 1.6 \times 10^{-3} \text{ A}$ or 1.6 mA or 0.0016 A.

cii). 7 Segment Display.

19 a). $\int_1^5 = 5.$

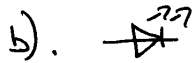

c). Protect LED from too much current/voltage.


20. a). AND gate



ii)

INPUT	OUTPUT
0	1
1	0

c i)

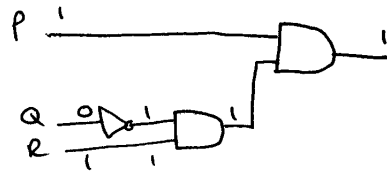

$P = 1$
 $Q = 0$
 $R = 1$

OR USE INFO TABLE!

c ii). Motor

21 a) Microphone

b). $G_{AM} = \frac{V_{out}}{V_{in}}$ how many times V_{out} is bigger than V_{in} .

c). 5000 Hz f does not change.

d). $P = \frac{E}{t} = \text{energy m / second} = \underline{150 \text{ Joules m / second}}$

22.

a). Process

b). Microphone.


bii). Loudspeakers

c).
$$G_{AV} = \frac{V_{out}}{V_{in}} = \frac{0.45}{0.15} = \underline{\underline{3}}$$



- Same frequency.
- Higher Amplitude.
- output V should be amplitude 5x bigger than the input.

~~23a)~~

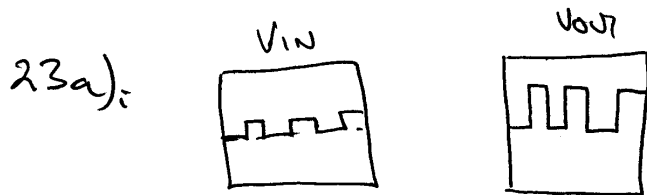

ii). digital.

b). Rodio.

Electronics CREDIT.

Credit

24. a) Loudspeakers

b). LED - does not have to produce much light
- does not use much energy.



ii).

$$R = \frac{V_R}{I}$$
$$V_R = 9 - 2.4$$
$$V_R = \underline{\underline{6.6V}}$$
$$R = \frac{6.6}{0.02}$$
$$R = \underline{\underline{330\Omega}}$$

25 a i) light \rightarrow electrical

ii).

$$V_2 = \frac{R_2}{R_1} \cdot V_1$$
$$V_2 = \frac{2400}{3000} \times 1.5$$
$$V_2 = \underline{\underline{1.2V}}$$

b i) Transistor

ii). 20 Lux

iii). Protect LED from too high a current (voltage,

Electronics CREDIT.

Credit

26 a) i).

NOT

LDR

ii)

	No Cam	Cam
LIGHT LDR	HIGH	LOW
R LDR	LOW	HIGH
V _{IN}	HIGH	LOW
V _{OUT}	LOW	HIGH

b) i).

Binary

Decimal.

ii)

AND.

00	0
01	00
10	00
11	1

iii)

Capacitor.

27 a) i


$$\frac{R_1}{R_2} = \frac{V_1}{V_2}$$

$$\frac{4300}{R_2} = \frac{4.3}{0.7}$$

$$\frac{4300}{R_2} = 6.143$$

$$R_2 = \frac{4300}{6.143}$$
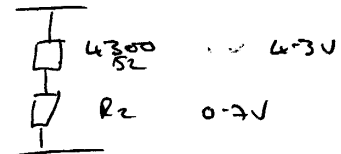
$$R_2 = \underline{\underline{700 \Omega}}$$



ii). **A** 80°C

B If $R_2 > 4300 \Omega$

so R_{TH} will have to \uparrow to get 0.7V.

\therefore Temp will decrease. [See curve!]

.7.

27b

i) Transistor


- ii).
- As Temp ↓ so $R_{thermistor} \uparrow$
 - $V_{across\ Thermistor} \uparrow$ to 0.7 or above
 - This voltage will switch on the transistor
 - Current flows through transistor + relay to switch on the heater.

(3)

28 a) a). $V_z = \frac{R_2}{R_1} \cdot V_s$

$V_z = \frac{15}{75} \times 5$

$V_z = \underline{\underline{0.1V}}$

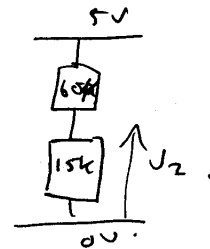

b. X - AND Y - OR.


iii).

PQ	R	S	T
00	0	0	0
01	0	0	0
10	0	0	0
11	1	0	1
00	0	1	1
01	0	1	1
10	0	1	1
11	1	1	1

$\frac{1}{2}$ each correct row.

iv). emergency exit.

29. a) AND

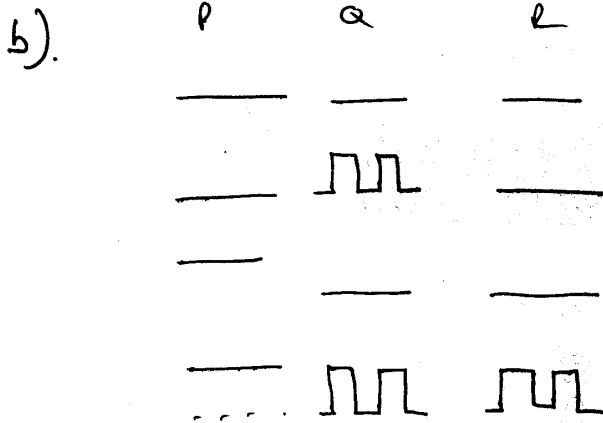

c) (i) Cap uncharged $V_C = 0$ $\xrightarrow{\text{NOT}}$ $V_Y = \text{HIGH}$
 Cap. charges $\gamma R \times$
 Cap charged $\gamma = \text{HIGH}$ $\xrightarrow{\text{NOT}}$ $V_Y = \text{LOW}$
 Cap discharges $\gamma R \gamma$.

(ii) \uparrow Resistance OR
 \uparrow Capacitance.

30

CREDIT.

Credit

a) Variable Resistor

b) Transistor

c) cool \rightarrow $R_{THERMISTOR} \downarrow \rightarrow$
 $V_{THERMISTOR} \downarrow$ (less 0.7V) \rightarrow
Transistor switched off LED off.

31. a) x = not gate

b)

	P	Q	R
overflow	0	1	0
acceptable	1	0	0
underfull	1	0	1


1 each row.

c) AND.

32. a) w, x

ii) \downarrow value \uparrow Resistor R + capacitor C .

b) $R_2 = \frac{V_R}{I} = \frac{(3-1.8)}{0.015} = \underline{\underline{80 \Omega}}$


33 a)  need the arrow plus
2 connecting links

b) i) 0.7V

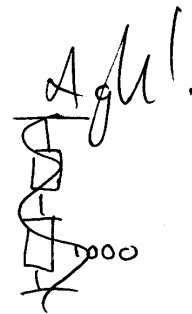ii) $V_R = 5 - 0.7 = \underline{\underline{4.3V}}$

iii)

$$R = \frac{V}{I} = \frac{4.3}{0.01} = \underline{\underline{430 \Omega}}$$




34 a). LDR.

b) i)

P	Q	R
0	0	0
0	1	0
1	0	0
1	1	1

ii) 5 eggs $A=1, C=1$.

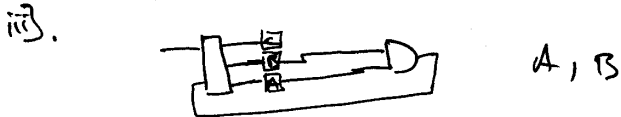

35. a). Transistor

b). loudspeaker

c). β Decreases

ii) ~~went~~ Resistance \downarrow $R \downarrow$ so V across $R \downarrow$

V across var. resistor \uparrow

When $V_{var} > 0.7$ transistor switched ON.

Current flows through L'speaker.

36 a). i LDR

ii)

	1P	2P	5P
P	0	1	0
Q	1	1	0
R	1	1	1
S	1	1	1

1 for each column.

b) A - NOT (B) AND

iii). $T \perp U \perp V \perp W \perp X \perp$

iv). solenoid.

37 a). Solar cell \rightarrow Amplifier \rightarrow Voltmeter.

Credit

b). i) $G_{AM} = \frac{V_{out}}{V_{in}} = \frac{40}{0.1} = \underline{\underline{400}}$

ii) $V_i = \frac{R_2}{R_1} \times V_s$ mixed up sign with R_1, R_2, V_i !

$$V_i = \frac{180}{400} \times 0.4$$

$$V_s = \underline{\underline{0.4 \text{ mV}}} \quad \text{Ⓢ}$$

$$V_i = \underline{\underline{0.18 \text{ mV}}}$$

38. a i). Power $G_{AM} = \frac{P_{out}}{P_{in}} = \frac{64}{16 \times 10^{-3}} = \underline{\underline{4000}}$

a ii). $P = \frac{V^2}{R}$

$$V^2 = P \cdot R$$

$$V^2 = 64 \times 9$$

$$V^2 = 576$$

$$V = \underline{\underline{24 \text{ V}}}$$

b). $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$

$$\frac{1}{R_p} = \frac{1}{9} + \frac{1}{9} = \frac{2}{9}$$
$$R_p = \underline{\underline{4.5 \Omega}}$$

c). 256 Hz .

CREDIT Electronics

Credit

39. a) Power Gain = $\frac{V_{out}}{V_{in}} = \frac{2}{5 \times 10^{-3}} = \underline{\underline{400}}$


a) $P = \frac{V^2}{R}$

$R = \frac{V^2}{P} = \frac{4^2}{2} = \underline{\underline{8 \Omega}}$

b). Push switch \rightarrow current thro coil. \rightarrow
magnetic field in coil attracts iron bar
to open door.

40 a). $V_{out} = GAIN \cdot V_{in}$
 $g = 150 \cdot V_{in}$
 $V_{in} = \frac{g}{150} = \underline{\underline{0.06V}}$

b) i).

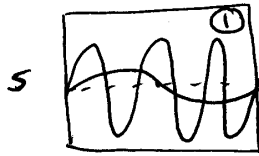

step 1 3 freq of string 5
draw 3 waves with $\textcircled{1}$
Greater amplitude [as louder] $\textcircled{1}$

ii). $\underline{\underline{196.0 \text{ Hz}}}$

