

- 1) B 1 A [current is the SAME IN SERIES]
- 2) B [R, S are the only resistors IN SERIES]
-

3 a i). 2

a ii). Live - Brown. Neutral - Blue.

b). $I = \frac{P}{V}$

$$I = \frac{460}{230}$$

$$I = \underline{\underline{2 \text{ A}}}$$

c i). 3 A.

c ii) Protect the flex of hair dryer from overheating.

4 a i). Brown

ii) Blue

iii) Earth

b). To stop Live + Neutral wires being pulled out of their pins, and causing a short circuit.

c). i). Double Insulation.

ii). Earth.

5 a). light

GENERAL

ii). heat

b i). Kettle or Food Processor.

ii). Green / Yellow.

iii). A 3A fuse. $P < 700 \text{ W}$.

B 13A fuse. $P > 700 \text{ W}$.

6 a) $P = I \cdot V$

$$0.3 = I \cdot 6$$

$$I = \frac{0.3}{6}$$

$$I = \underline{\underline{0.05 \text{ A}}}$$

b i). 


ii). A 230 V B Transformer

iii). Mains: ac direction of current continuously changes

Battery: dc direction of current is constant. (one direction).

7 a)

GENERAL

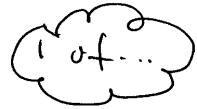

- Producing same amount of light as a filament bulb.
- Last $10\times$ longer as conventional lamps
- Cost 20p rather than $\pounds 1.00$ for the same time + same light

b). $100\text{ W: } \pounds 1 \times 365 = \pounds 365$
 $20\text{ W: } \pounds 0.20 \times 365 = \pounds 73$

$$\text{saving} = 365 - 73 = \underline{\underline{\pounds 292}}$$

c). a lower powered bulb (20 W) which uses less electrical energy produces the same amount of light as a higher powered bulb [100 W].

- d). i In the filament (wire)
ii In the gas.
-

8 a). $V = IR$
 $8.8 = 0.02 \times R$
 $R = \frac{8.8}{0.02}$
 $R = \underline{\underline{440\ \Omega}}$

b). $0.4\ \text{k}\Omega = \underline{\underline{400\ \Omega}}$

c i). Circuit 2 scale is too large. 0.2
The reading is too small for the scale.
It can only go up/down in 100's of Ohms.

c ii). ~~520~~ Turn dial to Ohms.

Using Electricity.

9 a i). $V = I R$
 $2 = I \cdot 8$
 $I = 0.25 \text{ A}$

GENERAL
 $I = ?$
 $R = 8$
 $V = 2$

a ii). $V_{\text{motor}} = 6 - 2 = \underline{\underline{4V}}$

b). $\downarrow R \rightarrow \uparrow \text{ current} \rightarrow \uparrow \text{ speed of motor.}$

c). Volume control, Light dimmer switch.

- 10
- CD/stereo on bath
 - could fall on + give person electric shock.
 - Too many appliances plugged into 1 socket.
 - adaptor could overheat \rightarrow Fire.
 - "Broken" flex insulation wrapped in tape.
 - wires could touch, short circuit + cause overheating + fire.
 - Vacuum cleaner is a **PHYSICAL** hazard rather than an Electrical hazard.

b). 12V

c) i). wire

ii). glass

iii). smaller than.

iv). smaller than.

12 ai)

	L1	L2	L3
I/A	0.3	0.3	0.3
V/V	12	12	12


a ii).

	L1	L2	L3
I/A	0.1	0.1	0.1
V/V	4V	4	4

b i) circuit (parallel)

b ii). Kettle; Electric Fire (appliance switch + socket switch).

13 a).

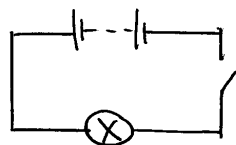


+| - = a cell

b). charge; current

c). electrical → light

d). To reflect light coming out of the back of the bulb forwards.

14. a)

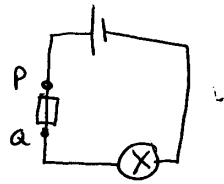

GENERAL

b).


Fuse put between P+a.

Bulb does not light

Because circuit is broken [by blown fuse]

If fuse was ok; circuit would be complete and bulb would be lit.

15 a).

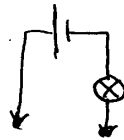

b).

connect probe ends together

circuit is complete

bulb lights.

c).

circuit is broken (wire / filament) so current cannot flow through it.

16 a). 230 V.

b).

Switch components on/off separately

All components are at same voltage [230V]

c i). $P_T = 4 \times 800 = 3200 \text{ W}$

ii). (A) kWh = $3.2 \times 3 = 9.6 \text{ kWh}$.

(B) cost = $5p \times 9.6 = 48p$.

d).

MCB - Miniature Circuit Breaker

(no mark given for TRP switch).

17 a)

b). S_2 by passes resistor so more current flows through the Motor.

c i). $kWh = 2 \times 8 = \underline{16 kWh.}$

c ii). $cost = ap \times 16 = 144p \quad [£1.44]$

18 a i). 

a ii). Earth wire

b). A: Brush.

B: Commutator.

C: Rotating Coil

D: Field Coil.

19 a i). It is double insulated.

ii). Line - Brown + Neutral - Blue

iii). 13A ($P > 700\text{ W}$).

b i).

$$I = \frac{V}{R}$$

$$R = 5000$$

$$V = 230$$

$$I = ?$$

$$I = \frac{230}{5000}$$

$$I = \underline{0.046\text{ A}}$$

b ii). Current is less than fuse value (13A)
Fuse would not melt/blow.

b iii). Protect flex of lawnmower.

b iv). Water will decrease the resistance
of the dummy so
current will increase.

20 a i) 4 A

a ii) $P = IV$

$$P = 4 \times 230$$

$$P = 920\text{ W}$$

$$V = 230 \text{ as "mains"}$$


b i). 10 A fuse (note 9 A at start)

b ii). To isolate (separate from mains)
appliance if there is a fault.

21 a i). wire ~~is~~ is moving in a magnetic field.

aii). loop wire into a coil (se)
more wire faster.

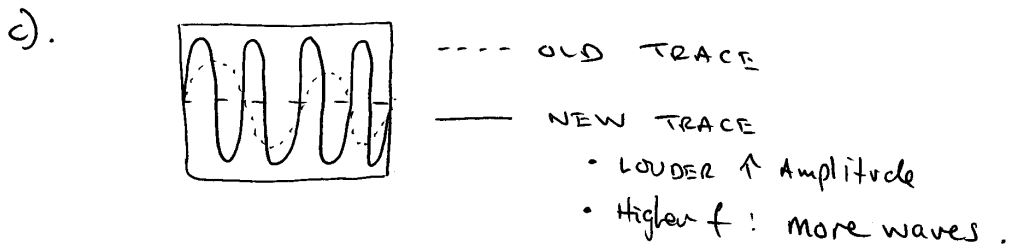b) $V_p = 2 \text{ squares} \times 0.2 \text{ mV} = \underline{\underline{0.4 \text{ mV}}}$



22 a i). 175Ω .

aii). $I = \frac{V}{R}$
 $I = \frac{230}{175}$
 $I = \underline{\underline{1.31 \text{ A}}}$

aiii). $P = I \cdot V$
 $P = 1.31 \times 230$ $\underline{\underline{300 \text{ W}}}$ lamp
 $P = \underline{\underline{301.3 \text{ W}}}$

b). In 1st 0.5s, resistance of the lamp is very low causing a high current to flow. This high current can overheat filament wire + melt it.


23 a). $I = P/V$

$$I = \frac{75 \times 10^{-3}}{3}$$

$$I = \underline{\underline{0.025 \text{ A}}} \quad (25 \text{ mA}).$$

b). 100 mA fuse.

24 a).

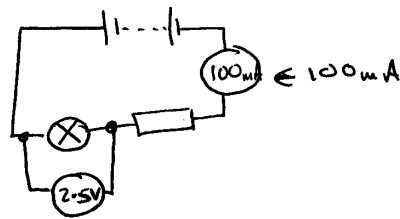

b i). $V_R = 12 - 2.5 = \underline{\underline{9.5 \text{ V}}}$

ii). $R = \frac{V_R}{I} = \frac{9.5}{0.1} = \underline{\underline{95 \Omega}}$

25 a). i $R = \frac{V}{I} = \frac{10}{1.2} = \underline{\underline{8.33 \Omega}}$

a ii). Resistance remains constant^① as graph shows straight line through zero^② so $I \propto V$.^①

$$I = 1.4 \text{ A} \rightarrow V = 11.6 \text{ V} \cdot \text{①}$$

$$R = \frac{11.6}{1.4} = 8.28 = \underline{\underline{8.3 \Omega}} \cdot \text{①}$$

Resistance remains constant^①

25 bi). graph is not a straight line.

b ii) **A** $I = 3.2 \text{ A}$

B $P = I \cdot V$
 $P = 3.2 \times 12$
 $P = \underline{\underline{38.4 \text{ W}}}$

26 ai). 230 V.

aii). parallel.

b).

$$I = \frac{P}{V}$$

$$P = 110 + 22 + 20 + 18$$

$$P = 170 \text{ W}$$

$$I = \frac{170}{230}$$

$$I = 0.73913 \text{ A}$$

$$I = \underline{\underline{0.74 \text{ A}}}$$

c).

$$P = \frac{V^2}{R}$$

$$110 = \frac{230^2}{R}$$

$$R = \frac{52900}{110}$$

$$R = \underline{\underline{481 \Omega}}$$

or calc I from $I_{\text{rms}} = \frac{P_{\text{av}}}{V}$

then $V = \frac{I R_{\text{rms}}}{I_{\text{rms}}}$

(480.909090 ...)

d). To protect cable & adaptor from overheating.

$$27 \text{ a) } R = \frac{V}{I}$$

$$R = \frac{3.0}{0.10}$$

$$R = \underline{\underline{30 \Omega}}$$


a ii). 0.10 A (in series !)

b i). Variable Resistor resistance is lowered[⊙]
in steps of 0.05 A on the ammeter

b ii). Result no. 4[⊙] because voltage did not
increase by 1.5 V .[⊙]

c). The resistance is constant.

28 a).

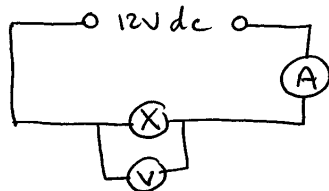

b). Resistance.

c i). $IV = 24$. $I^2 R = 24$.

ii) Power

iii) Watts.

29 a). 3A

b). $V_x = IR_x$

$V_x = 3 \times 2$

$V_x = \underline{\underline{6V}}$

c). $R_y = \frac{V_y}{I}$ ⑤

$V_y = 36 - 12 - 6$

$V_y = \underline{\underline{18V}}$ ①

$R_y = \frac{18}{3}$ ②

$R_y = \underline{\underline{6\Omega}}$ ①

d). In parallel, the total resistance of bulbs decreases.

30 a). sidelights

b). no current through relay coil
 opens relay switch to switch off Headlights.
 Side lights own connection to battery.

$$c). i). I = \frac{P}{V} = \frac{(4 \times 6)}{12} = \frac{24}{12} = \underline{\underline{2A}}$$

$$ii). Q = I \cdot t = 2 \times (10 \times 60) = 2 \times 600 = \underline{\underline{1200C}}$$

iii). Headlights have a higher power rating
 so change more electrical energy \rightarrow light.

Using Electricity.

31 a). D

$$\text{b) i) } \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_p} = \frac{1}{8} + \frac{1}{4} + \frac{1}{4}$$

$$\frac{1}{R_p} = \frac{1+2+2}{8} = \frac{5}{8}$$

$$R_p = \frac{8}{5} = \underline{\underline{1.6 \Omega}}$$

bii).

$$I = \frac{V}{R}$$

$$I = \frac{12}{1.6}$$

$$I = \underline{\underline{7.5 \text{ A}}}$$

c). Brighter \rightarrow let more current through
 \rightarrow lower bulb resistance.
 \Rightarrow lower circuit resistance.

32 a i). Y

aii). Reduce costs of wiring

Can use thinner wires

Use lower currents in wires - safer.

b).

Lighting fuse lower (5A) as only bulbs are connected to it. Ring circuits can connect higher power devices.

LIVE + NEUTRAL wires are split in a ring circuit to half the drawn current in each wire.

Lighting circuit wires are not as they only carry "low" currents.

c i) High Power rating - draws a high current from the mains.

$$\text{cii). } E = P \cdot t = 2200 \times [2 \times 60 \times 60]$$

$$E = 15840000 \text{ J.}$$

$$E = 15.84 \cdot 10^6 \text{ J.}$$

di). Safety device.

ii). Live wire loose + contacts case. /

• [shorts with case]

Case live

• High current flows to earth +

• Blows fuse

• Appliance Isolated

33 a i). To isolate house from the mains.

a ii). RING circuit (B) LIGHTING circuit (E)

a iii). In ring circuit: there are 2 LIVE WIRES and 2 NEUTRAL wires, 2 paths in + 2 paths out for the current.

b i).

$$P = \frac{V^2}{R}$$

$$25 = \frac{230^2}{R}$$

$$R = \frac{52900}{25}$$

$$R = \underline{\underline{2116 \Omega}}$$

b ii).

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$\frac{1}{R_p} = \frac{1}{2116} + \frac{1}{2116} + \frac{1}{2116} + \frac{1}{2116}$$

$$\frac{1}{R_p} = \frac{4}{2116}$$

$$R_p = \frac{2116}{4} \quad \Omega$$

$$R_p = \underline{\underline{529 \Omega}}$$

34 a i) can be re-set.

a ii). current through coil produces a magnetic field

- when current is too high magnetic field is strong enough to pull iron contact across

- This breaks the circuit

- No current can now flow.

b i).

$$P = \frac{V^2}{R}$$

$$60 = \frac{230^2}{R}$$

$$R = \frac{52900}{60}$$

$$R = \underline{\underline{882 \Omega}}$$

$$P = 60 \text{ W}$$

$$V = 230 \text{ V}$$

$$I = \text{NOT GIVEN}$$

$$R = ?$$

b ii).

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_p} = \frac{1}{882} + \frac{1}{882} + \frac{1}{882} \quad (\text{ol.})$$

$$\frac{1}{R_p} = \frac{3}{882}$$

$$R_p = \frac{882}{3}$$

$$R_p = \underline{\underline{294 \Omega}}$$

$$P = \frac{V^2}{R}$$

$$(3 \times 60) = \frac{230^2}{R}$$

$$180 = \frac{52900}{R}$$

$$R = \underline{\underline{294 \Omega}}$$

Using Electricity.

34 biii). $P = I \cdot V$

$$[3760] = I \cdot 230$$

$$I = \frac{3760}{230}$$

$$I = 0.78 \text{ A}$$

\therefore MCB will NOT
switch off.

35 a). • change direction of the current
[swap battery round].

• change direction of magnetic field
[swap poles of magnets round].

b). i (A) Field coil (B) Commutator.

ii). (A) To produce a more constant force
acting on the brush which gives a smoother turning effect. (oe)

(B) Stronger magnetic field can be produced
They are lighter (for same mag. field)
Magnetic field can be switched off.

